



2018 VI 11

1430

Seat No. :

--	--	--	--	--

Time : 2 Hours

DIGITAL ELECTRONICS AND COMPUTERS

Subject Code

V	3	3	1
---	---	---	---

Total No. of Questions : 5

(Printed Pages : 3)

Maximum Marks : 50

- INSTRUCTIONS:** i) Answer **each** question on a fresh page.  
ii) Write the number of question and sub-question clearly.  
iii) **All** questions are **compulsory**.  
iv) Figures to the right indicate full marks.  
v) Draw neat diagrams **wherever** necessary.

1. A) Fill in the blanks. [2]

i) The decimal equivalent of  $(F)_{16}$  is \_\_\_\_\_

ii) When input signals  $A = 1$  and  $B = 0$  is applied to an EX-NOR gate, its output signal will be \_\_\_\_\_

B) Answer the following :

i) With a neat circuit diagram, explain 4-bit ring counter. [3]

ii) What are bubbled gates ? With the help of logic symbol and truth table, explain bubbled OR gate. [3]

C) Answer the following : [2]

What is shift register ? Draw a neat circuit diagram of 4-bit shift right register.

2. A) Define the following : [2]

i) Full Adder

ii) Buffer Register.



B) Answer the following :

- i) Draw a neat circuit diagram of JK flip flop and explain its 'Reset' mode. [3]
- ii) Explain the terms 'volatile memory' and 'non-volatile memory'. Give one example of each. [3]

C) Answer the following :

Draw the block diagram of counter type analog to digital converter. [2]

3. A) Fill in the blanks: [2]

- i) The 1's complement of binary number  $(1010)_2$  is \_\_\_\_\_
- ii) The 8080A microprocessor consists of \_\_\_\_\_ number of functional chips.

B) Do as directed : [3]

- i) Convert  $(4429)_{10}$  to its octal equivalent.
- ii) Convert  $(101100010)_2$  to its decimal equivalent
- iii) Convert  $(1993)_{10}$  to its hexadecimal equivalent.

C) Answer the following in detail :

Draw a diagram of typical microprocessor and state the functions of Arithmetic Logic Unit (ALU). [5]

OR

Draw a block diagram of computer system state any three functions of Central Processing Unit (CPU). [5]

4. A) Answer the following in **one** sentence. [2]

- i) What is the clock frequency of 8085 microprocessor ?
- ii) Write the formula to obtain total time period of the output waveform of a symmetrical astable multivibrator.



B) Answer the following :

State Demorgan's second theorem. Show that  $\overline{A \cdot B} = \overline{A} + \overline{B}$ . [3]

C) Answer the following in detail :

Explain 'Mouse' as an input device and 'Plotter' as an output device in the computer system. [5]

OR

Explain 'Floppy disk' as storage device, state the diameters of mini-floppy and micro-floppy. [5]

5. Answer the following :

i) Draw neat logic diagrams converting a NOR gate to AND gate and OR gate. [2]

ii) State any two uses of 'Schmitt Trigger'. [2]

iii) Differentiate between 'edge triggering' and 'level clocking' with two points of difference in flip-flops. [2]

iv) With the help of logic symbol, explain 'multiplexer'. [2]

v) State any two advantages of binary ladder. [2]

---